

## Fleet Multi-Temp Quiz 5

Name: \_\_\_\_\_ Number Correct: \_\_\_\_\_/10

### Multiple Choice

Identify the choice that best completes the statement or answers the question.  
This quiz should take approximately 15 minutes to complete.

1. If resistance is increased in a circuit with constant source voltage:
  - a. Current flow stops.
  - b. Amperage increases.
  - c. Amperage decreases.
  - d. Voltage always stays the same.
2. Electrical pressure is \_\_\_\_\_ and electrical flow is \_\_\_\_\_.
  - a. Amps, volts.
  - b. Volts, amps.
  - c. Resistance, amps.
  - d. Amps, resistance.
3. Which of the following is an electromagnetic device?
  - a. Relay
  - b. Solenoid
  - c. Alternator
  - d. All of the above.
4. Which component controls high amp circuits with low amp control?
  - a. Microprocessor
  - b. Alternator
  - c. Switch
  - d. Relay
5. The \_\_\_\_\_ provides voltage spike protection for electromagnetic devices.
  - a. Fuse
  - b. Circuit breaker
  - c. Arc suppression diode
  - d. Microprocessor
6. Which meter requires the component to be electrically disconnected before taking the reading?
  - a. Voltmeter
  - b. Ammeter
  - c. Manometer
  - d. Ohmmeter

7. To create, or induce, voltage, you must have:
  - a. A magnetic field, a conductor and movement between the two.
  - b. A magnetic field, a conductor and stationary windings.
  - c. Two conductors and movement between them.
  - d. A conductor and a collapsing magnetic field.
8. The voltage regulator controls alternator output by controlling voltage into the:
  - a. Stator winding.
  - b. Capacitor plates.
  - c. Regulator.
  - d. Field winding.
9. When diagnosing an alternator that does not charge:
  - a. Replace the alternator harness because the resistor is broken.
  - b. Check for voltage at the 2A, D+, and AC tap terminals at the alternator.
  - c. Check for voltage on the output, sense and excite terminals at the alternator.
  - d. Replace the F15 fuse on the relay board.
10. Which of the following alternator terminals is used by the voltage regulator to determine the battery's level of charge?
  - a. B+
  - b. EXC
  - c. SEN
  - d. FLD